


E15 Processor

Machine language

bin	hex
100100100000	920
100100010001	911
101001100000	a60
111100100111	f27
001100001110	30e
000000000000	000

Machine language		Assembly language
bin	hex	
100100100000	920	{movi, RXX, Rg2, 4'b0000}
100100010001	911	{movi, RXX, Rg1, 4'b0001}
101001100000	a60	{add, Rg1, Rg2, 4'b0000}
111100100111	f27	{cmpi, RXX, Rg2, 4'b0111}
001100001110	30e	{jnz, RXX, RXX, 4'b1110}
000000000000	000	{jmp, RXX, RXX, 4'b0000}

100100100000

 

{movi, RXX, Rg2, 4'b0000}

4-bit opcode

2-bit source
register

2-bit
destination
register

4-bit immediate
value

This E15 assembly language....

```
{movi, RXX, Rg2, 4'b0000}  
{movi, RXX, Rg1, 4'b0001}  
{add,  Rg1, Rg2, 4'b0000}  
{cmpi, RXX, Rg2, 4'b0111}  
{jnz,  RXX, RXX, 4'b1110}  
{jmp,  RXX, RXX, 4'b0000}
```

... corresponds (roughly) to the following pseudocode:


```
int rg2 = 0;  
int rg1 = 1;  
while (true) {  
    rg2 += rg1;  
    if (rg2 == 7)  
        break;  
}  
while (true) {}
```

E15 instruction set

<code>jmp</code>	<code>= 4'b0000,</code>	jump
<code>jz</code>	<code>= 4'b0010,</code>	jump if zero
<code>jnz</code>	<code>= 4'b0011,</code>	jump if not zero
<code>movi</code>	<code>= 4'b1001,</code>	move immediate
<code>mov</code>	<code>= 4'b1000,</code>	move
<code>addi</code>	<code>= 4'b1011,</code>	add immediate
<code>add</code>	<code>= 4'b1010,</code>	add
<code>subi</code>	<code>= 4'b1101,</code>	subtract immediate
<code>sub</code>	<code>= 4'b1100,</code>	subtract
<code>cmpi</code>	<code>= 4'b1111,</code>	compare immediate
<code>cmp</code>	<code>= 4'b1110;</code>	compare

```
jmp  = 4'b0000,  
    Add the given immediate value to the program counter  
jz   = 4'b0010,  
    Add the given immediate value to the program counter if the ZERO flag is true  
jnz  = 4'b0011,  
    Add the given immediate value to the program counter if the ZERO flag is  
    false  
movi = 4'b1001,  
    Move the given immediate value into the given destination  
mov  = 4'b1000,  
    Move the given source register value into the given destination  
addi = 4'b1011,  
    Add the given immediate value into the given destination  
add  = 4'b1010,  
    Add the given source register value into the given destination  
subi = 4'b1101,  
    Subtract the given immediate value from the given destination  
sub  = 4'b1100,  
    Subtract the given source register value from the given destination  
cmpi = 4'b1111,  
    Compare the given immediate value to the given destination register and set  
    the ZERO flag accordingly  
cmp  = 4'b1110;  
    Compare the given source register value to the given destination register and  
    set the ZERO flag accordingly
```

A tour of the E15 opcodes

 

A tour of the E15 opcodes

jmp

jnz

jz

add

sub

subi

addi

cmp


cmpi

mov


movi

These are *arithmetic instructions*.
They all take two operands.
These instructions will set the zero flag to correspond to the result of the operation, i.e. if the operands' sum or difference is zero, the zero flag is set to one (true).


A tour of the E15 opcodes

 


A tour of the E15 opcodes

 

A tour of the E15 opcodes

 

A tour of the E15 opcodes

 

What's inside the E15 processor?

4 general-purpose registers

Rg0 (4-bit)

Rg1 (4-bit)

Rg2 (4-bit)

Rg3 (4-bit)

program
counter (4-bit)

zero flag (1-bit)

zFlag

instruction memory (16 x 12-bit)

myRom[0] (12-bit)

myRom[1] (12-bit)

myRom[2] (12-bit)

myRom[3] (12-bit)

myRom[4] (12-bit)

myRom[5] (12-bit)

myRom[6] (12-bit)

myRom[7] (12-bit)

myRom[8] (12-bit)

myRom[9] (12-bit)

myRom[10] (12-bit)

myRom[11] (12-bit)

myRom[12] (12-bit)

myRom[13] (12-bit)

myRom[14] (12-bit)


myRom[15] (12-bit)

Here's a more complicated E15 program. What does it do?

```
/*          OPCODE SRC  DST  IMMDATA */
myROM[0] = {movi, RXX, Rg1, 4'b0011};
myROM[1] = {add,  Rg1, Rg1, 4'b0000};
myROM[2] = {add,  Rg1, Rg1, 4'b0000};
myROM[3] = {movi, RXX, Rg2, 4'b1100};
myROM[4] = {cmp,  Rg1, Rg2, 4'b0000};
myROM[5] = {jz,   RXX, RXX, 4'b0011};
myROM[6] = {movi, RXX, Rg2, 4'b0001};
myROM[7] = {jmp,  RXX, RXX, 4'b0000};
myROM[8] = {movi, RXX, Rg2, 4'b0000};
myROM[9] = {jmp,  RXX, RXX, 4'b0000};
myROM[10] = {jmp, RXX, RXX, 4'b0000};
myROM[11] = {jmp, RXX, RXX, 4'b0000};
myROM[12] = {jmp, RXX, RXX, 4'b0000};
myROM[13] = {jmp, RXX, RXX, 4'b0000};
myROM[14] = {jmp, RXX, RXX, 4'b0000};
myROM[15] = {jmp, RXX, RXX, 4'b0000};
```

Note that we assign instruction values to all 16 ROM cells, not just those that our program will actually use.


How does a program execute?

 

Initially, the program counter is zero and the ROM contains our program. Other registers have unknown values.

instruction memory (16 x 12-bit)	
0	{movi, RXX, Rg1, 4'b0011}
1	{add, Rg1, Rg1, 4'b0000}
2	{add, Rg1, Rg1, 4'b0000}
3	{movi, RXX, Rg2, 4'b1100}
4	{cmp, Rg1, Rg2, 4'b0000}
5	{jz, RXX, RXX, 4'b0011}
6	{movi, RXX, Rg2, 4'b0001}
7	{jmp, RXX, RXX, 4'b0000}
8	{movi, RXX, Rg2, 4'b0000}
9	{jmp, RXX, RXX, 4'b0000}
10	{jmp, RXX, RXX, 4'b0000}
11	{jmp, RXX, RXX, 4'b0000}
12	{jmp, RXX, RXX, 4'b0000}
13	{jmp, RXX, RXX, 4'b0000}
14	{jmp, RXX, RXX, 4'b0000}
15	{jmp, RXX, RXX, 4'b0000}

How does a program execute?

 

How does a program execute?

zero flag (1-bit)

?

4 general-purpose registers

Rg0

?

Rg1

?

Rg2

?

Rg3

?

{movi, RXX, Rg1, 4'b0011}


program counter

0000


instruction memory (16 x 12-bit)

0	{movi, RXX, Rg1, 4'b0011}
1	{add, Rg1, Rg1, 4'b0000}
2	{add, Rg1, Rg1, 4'b0000}
3	{movi, RXX, Rg2, 4'b1100}
4	{cmp, Rg1, Rg2, 4'b0000}
5	{jz, RXX, RXX, 4'b0011}
6	{movi, RXX, Rg2, 4'b0001}
7	{jmp, RXX, RXX, 4'b0000}
8	{movi, RXX, Rg2, 4'b0000}
9	{jmp, RXX, RXX, 4'b0000}
10	{jmp, RXX, RXX, 4'b0000}
11	{jmp, RXX, RXX, 4'b0000}
12	{jmp, RXX, RXX, 4'b0000}
13	{jmp, RXX, RXX, 4'b0000}
14	{jmp, RXX, RXX, 4'b0000}
15	{jmp, RXX, RXX, 4'b0000}


How does a program execute?

 


How does a program execute?

 


How does a program execute?

 


How does a program execute?

 


How does a program execute?

 


How does a program execute?

 


How does a program execute?

 


How does a program execute?

 


How does a program execute?

 


How does a program execute?

 


How does a program execute?

 


How does a program execute?

 


How does a program execute?

 

How does a program execute?

 

How does a program execute?

 

We can now understand this E15 program in terms of (roughly) equivalent pseudocode.

```
/*          OPCODE SRC  DST  IMMDATA */
myROM[0] = {movi, RXX, Rg1, 4'b0011};
myROM[1] = {add,  Rg1, Rg1, 4'b0000};
myROM[2] = {add,  Rg1, Rg1, 4'b0000};
myROM[3] = {movi, RXX, Rg2, 4'b1100};
myROM[4] = {cmp,  Rg1, Rg2, 4'b0000};
myROM[5] = {jz,   RXX, RXX, 4'b0011};
myROM[6] = {movi, RXX, Rg2, 4'b0001};
myROM[7] = {jmp,  RXX, RXX, 4'b0000};
myROM[8] = {movi, RXX, Rg2, 4'b0000};
myROM[9] = {jmp,  RXX, RXX, 4'b0000};
myROM[10] = {jmp,  RXX, RXX, 4'b0000};
myROM[11] = {jmp,  RXX, RXX, 4'b0000};
myROM[12] = {jmp,  RXX, RXX, 4'b0000};
myROM[13] = {jmp,  RXX, RXX, 4'b0000};
myROM[14] = {jmp,  RXX, RXX, 4'b0000};
myROM[15] = {jmp,  RXX, RXX, 4'b0000};
```

```
int rg1 = 3;
rg1 += rg1;
rg1 += rg1;
int rg2 = 12;
if (rg1==rg2)
    rg2 = 0;
else
    rg2 = 1;
while (true) {}
```

Overflow

Consider this E15 program:

```
myROM[0] = {movi, RXX, Rg0, 4'b0000}; // Rg0 = 0;  
myROM[1] = {movi, RXX, Rg1, 4'b1111}; // Rg1 = 15;  
myROM[2] = {subi, RXX, Rg0, 4'b0001}; // Rg0 = Rg0 - 1;  
myROM[3] = {addi, RXX, Rg1, 4'b0001}; // Rg1 = Rg1 + 1;  
myROM[4] = {jmp, RXX, RXX, 4'b0000}; // end program
```

What will be the final value of Rg0?

What will be the final value of Rg1?

Keep in mind that these are each 4-bit registers.

Overflow

```
myROM[0] = {movi, RXX, Rg0, 4'b0000}; // Rg0 = 0;  
myROM[1] = {movi, RXX, Rg1, 4'b1111}; // Rg1 = 15;  
myROM[2] = {subi, RXX, Rg0, 4'b0001}; // Rg0 = Rg0 - 1;  
myROM[3] = {addi, RXX, Rg1, 4'b0001}; // Rg1 = Rg1 + 1;  
myROM[4] = {jmp, RXX, RXX, 4'b0000}; // end program
```


E15 uses the usual algorithm for binary addition when adding and subtracting registers. In the case of subtraction, we must recall that subtraction is defined as addition of a negative.

In both cases the result must fit in four bits!

Calculating the final value of Rg0

$$\begin{array}{r} 0000 \\ - 0001 \\ \hline \end{array}$$

????

 
$$\begin{array}{r} 0000 \\ + 1111 \\ \hline \end{array}$$

????

Calculating the final value of Rg1

$$\begin{array}{r} 1111 \\ + 0001 \\ \hline \end{array}$$

????

Overflow

```
myROM[0] = {movi, RXX, Rg0, 4'b0000}; // Rg0 = 0;  
myROM[1] = {movi, RXX, Rg1, 4'b1111}; // Rg1 = 15;  
myROM[2] = {subi, RXX, Rg0, 4'b0001}; // Rg0 = Rg0 - 1;  
myROM[3] = {addi, RXX, Rg1, 4'b0001}; // Rg1 = Rg1 + 1;  
myROM[4] = {jmp, RXX, RXX, 4'b0000}; // end program
```

E15 uses the usual algorithm for binary addition when adding and subtracting registers. In the case of subtraction, we must recall that subtraction is defined as addition of a negative.

In both cases the result must fit in four bits!

Calculating the final value of Rg0

$$\begin{array}{r} 0000 \\ - 0001 \\ \hline 1111 \end{array}$$

equivalent

$$\begin{array}{r} 0000 \\ + 1111 \\ \hline 1111 \end{array}$$

Subtracting 1 is
the same as adding -1

Calculating the final value of Rg1

$$\begin{array}{r} 1111 \\ + 0001 \\ \hline 0000 \end{array}$$

This addition produces
a carry-out bit, which
we ignore.

Overflow

Calculating the final value of Rg0

$$\begin{array}{r} 0000 \\ - 0001 \\ \hline 1111 \end{array}$$

equivalent

$$\begin{array}{r} 0000 \\ + 1111 \\ \hline 1111 \end{array}$$

Calculating the final value of Rg1

$$\begin{array}{r} 1111 \\ + 0001 \\ \hline 0000 \end{array}$$

This is the phenomenon of *wraparound*.

E15 registers are 4-bit. This means they can store unsigned decimal values between 0 and 15, inclusive.

Because numbers are confined to a fixed bit width, adding or subtracting beyond the expressible range will cause the value to "wrap":

- too large values (such as $15+1=16$) will become small (here, 0)
- too small values (such as $0-1=-1$) will become large (here, 15)

The extreme ends of the number line connect.

Overflow

```
.....  
myROM[12] = {addi, RXX, Rg0, 4'b0011}; // Rg0 += 3;  
myROM[13] = {addi, RXX, Rg0, 4'b0011}; // Rg0 += 3;  
myROM[14] = {addi, RXX, Rg0, 4'b0011}; // Rg0 += 3;  
myROM[15] = {addi, RXX, Rg0, 4'b0011}; // Rg0 += 3;
```

Now consider this partial program. We show only the last four instructions, occupying addresses 12 through 15. What will happen *after* the instruction at address 15 executes?

- Program stops?
- Crash?
- Error message?
- Go back to beginning, at address 0?
- Go to address 16?

Remember, the E15 memory unit has only 16 cells, numbered 0 through 15.

Overflow

```
.....  
myROM[12] = {addi, RXX, Rg0, 4'b0011}; // Rg0 += 3;  
myROM[13] = {addi, RXX, Rg0, 4'b0011}; // Rg0 += 3;  
myROM[14] = {addi, RXX, Rg0, 4'b0011}; // Rg0 += 3;  
myROM[15] = {addi, RXX, Rg0, 4'b0011}; // Rg0 += 3;
```

Now consider this partial program. We show only the last four instructions, occupying addresses 12 through 15. What will happen *after* the instruction at address 15 executes?

Calculating the next value of program counter

1111	=15
+ 0001	increment

0000	=new pc

Therefore, the program continues executing at address 0.
That's why we need to explicitly mark the end of the program with a `{jmp, RXX, RXX, 4'b0000}` instruction!
Remember the the program counter is a 4-bit register, just like the others.

E15 in Verilog

Let's look at some interesting parts of the (incomplete) single-cycle E15 implementation in Verilog.

You can follow along in the source code you've been given.

```
module simpleALU(  
    input addNotSub,  
    input [3:0] src, dst,  
    output zFlag,  
    output [3:0] res);  
    wire Cout;  
  
    fourbit_adder the_adder(dst, addNotSub ? src : ~src,  
        ~addNotSub, res, Cout);  
  
    assign zFlag = !(res);  
  
endmodule
```

Before we get into the E15 processor itself, let's define an ALU module.

This ALU supports only two operations: add and subtract. The addNotSub input selects the operation.

```
module simpleALU(  
    input addNotSub,  
    input [3:0] src, dst,  
    output zFlag,  
    output [3:0] res);  
    wire Cout;  
  
    fourbit_adder the_adder(dst, addNotSub ? src : ~src,  
        ~addNotSub, res, Cout);  
  
    assign zFlag = !(res);  
  
endmodule
```

We use our **fourbit_adder** module to do the math for us. Note that for subtraction, we invert the second operand and add one via **Cin**, exactly as we previously discussed how subtractors work. The result is passed out in **res**.

```
module simpleALU(  
    input addNotSub,  
    input [3:0] src, dst,  
    output zFlag,  
    output [3:0] res);  
    wire Cout;  
  
    fourbit_adder the_adder(dst, addNotSub ? src : ~src,  
        ~addNotSub, res, Cout);  
  
    assign zFlag = !(res);  
  
endmodule
```

The ALU's **zFlag** output will be set to 1 when the result of the arithmetic operation is zero. We use the logical not operator **!** to do this.

```
simpleALU dataALU(addNotSub, operand1, operand2,  
    aluOutputZero, aluOutput);  
simpleALU pcALU(1'b1, pc, pcIncr, pcz, pcRes);
```

The E15 processor contains
not one, but *two* ALUs: **dataALU**
and **pcALU**.

```
// Register names
parameter
    Rg0 = 2'b00, Rg1 = 2'b01,
    Rg2 = 2'b10, Rg3 = 2'b11,
    RXX = 2'b00;

// Opcodes
parameter
    jmp  = 4'b0000, jz    = 4'b0010,
    movi = 4'b1001, mov   = 4'b1000,
    addi = 4'b1011, add   = 4'b1010,
    subi = 4'b1101, sub   = 4'b1100,
    cmpi = 4'b1111, cmp   = 4'b1110,
    jnz  = 4'b0011;
```

Now here's the E15 processor itself.

We're given values of constant symbols used in E15 assembly code. The Verilog **parameter** syntax is similar to C++ **const**, in that for convenience we are simply giving a name to a numeric value.

For example, the symbol **subi** maps to the 4-bit value 1101.

```
/*Processor state*/  
reg [3:0] pc;                // Program Counter  
reg      zFlag;              // Zero flag  
reg [3:0] r0, r1, r2, r3;    // Registers  
  
/*Program storage*/  
reg [11:0] myROM [15:0], myROM (holds program)
```

Here we define the mutable storage capacity of the processor: the program counter, the zero flag, the four general-purpose registers, and the instruction memory (ROM).

Note that these components correspond to the elements described in the slide titled
"What's inside the E15 processor?"

```
/*Processor state*/  
reg [3:0] pc;                // Program Counter  
reg      zFlag;              // Zero flag  
reg [3:0] r0, r1, r2, r3;    // Registers  
  
/*Program storage*/  
reg [11:0] myROM [15:0];     // ROM (holds program)
```

The syntax defining **myROM** is worth discussing.

myROM is an array of 16 elements.
Each element is a 12-bit value
(i.e. one instruction).

Therefore **myROM[0]** is the first instruction of our program.
myROM[0][0] is the MSB of the first instruction.


```
initial
begin

    `include "program1.v"
    // load the program

    pc = 4'b0000;
    // initialize the program counter

end
```

This code is run when the processor is "turned on." Here we set the initial value of registers.

The include line brings in an external file where our program is stored. That code in turn will assign values to each element of the **myROM** array. After this **myROM** will never change

Then, we initialize our program counter to zero, the address of the first instruction.

Other registers (**Rg0**, **Rg1**, **Rg2**, **Rg3**, **zFlag**) are not initialized and have no defined initial value.

```
/*Parts of the instruction*/  
wire [3:0] opCode;           // op code  
wire [1:0] src, dst;         // src and dst register  
wire [3:0] immData;          // "Immediate" data  
  
assign {opCode, src, dst, immData} = myROM[pc];
```

Here we define wires corresponding to each field of an instruction.

The opcode is 4 bits, the source and destination register names are 2 bits each, and the immediate data field is four bits.

The **assign** statement accesses the program memory, retrieving the instruction pointed to by the program counter. Then we map that value to each of the four fields.

Because this is *continuous assignment*, the field wires are updated whenever the program counter is changed.

```
always @(posedge clk)
begin
```

```
    // Update zero flag
    case(opCode)
        addi, add, subi, sub, cmpi, cmp:
            begin
                zFlag <= aluOutputZero;
            end
    endcase
```

```
    // update destination register
    case(opCode)
        movi, mov, add, addi, sub, subi:
            case(dst)
                Rg0: r0 <= storeVal;
                Rg1: r1 <= storeVal;
                Rg2: r2 <= storeVal;
                Rg3: r3 <= storeVal;
            endcase
    endcase
```

```
    // Update program counter
    pc <= pcRes;
```

```
end
```

This is the heart of the processor.
This code defines a loop that executes
at every clock cycle.

```

always @(posedge clk)
    begin

        // Update zero flag
        case(opCode)
            addi, add, subi, sub, cmpi, cmp:
                begin
                    zFlag <= aluOutputZero;
                end
            endcase

        // update destination register
        case(opCode)
            movi, mov, add, addi, sub, s
                case(dst)
                    Rg0: r0 <= storeVal;
                    Rg1: r1 <= storeVal;
                    Rg2: r2 <= storeVal;
                    Rg3: r3 <= storeVal;
                endcase
            endcase

        // Update program counter
        pc <= pcRes;

    end

```

Here, we need to save the ALU's zero flag output for those instructions that set it.

The **case** syntax lets us provide conditional actions for certain opcodes, similar to C++'s **switch**.

```

always @(posedge clk)
    begin

        // Update zero flag
        case(opCode)
            addi, add, subi, sub, cmpi, cmp:
                begin
                    zFlag <= aluOutputZero;
                end
            endcase

        // update destination register
        case(opCode)
            movi, mov, add, addi, sub, subi:
                case(dst)
                    Rg0: r0 <= storeVal;
                    Rg1: r1 <= storeVal;
                    Rg2: r2 <= storeVal;
                    Rg3: r3 <= storeVal;
                endcase
            endcase

        // Update program counter
        pc <= pcRes;

    end

```

Then, we need to update the destination register for those instructions that set it. Depending on the value of the **dst** field, we will assign **storeVal** to one of the four general-purpose registers.

Note that other instructions, such as **cmp** and **jmp**, do not modify these registers.

```

always @(posedge clk)
begin

    // Update zero flag
    case(opCode)
        addi, add, subi, sub, cmpi, cmp:
            begin
                zFlag <= aluOutputZero;
            end
    endcase

    // update destination register
    case(opCode)
        movi, mov, add, addi, sub, subi:
            case(dst)
                Rg0: r0 <= storeVal;
                Rg1: r1 <= storeVal;
                Rg2: r2 <= storeVal;
                Rg3: r3 <= storeVal;
            endcase
    endcase

    // Update program counter
    pc <= pcRes;

end


```

Finally, we update the program counter with the new value calculated by pcALU.


After that, the clock cycle is finished and we move on to the next instruction.

E15 multicycle

E15 Processor

 

Single Cycle, Multi-Cycle, Vs. Pipeline

 

What happens in each cycle? E15

fetch

opcode, src, dst, immData <= myROM[pc]

decode

mBus <= sourceValue1

dBus <= sourceValue2

addNotSub <= addOrSubtract?

exec

pcIncr <= nextInstruction

mBus <= aluResult

store

destinationValue <= mBus

pc <= pc + pcIncr